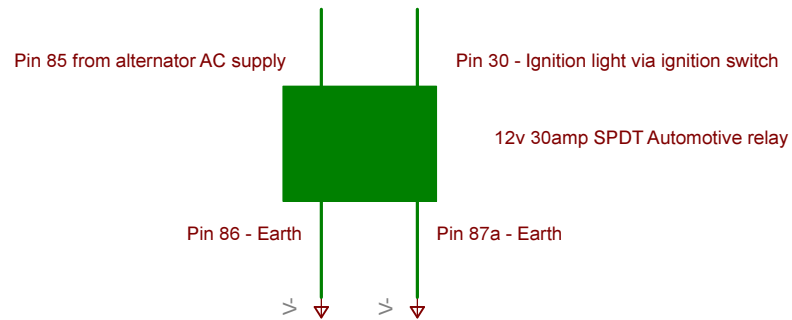


Alternator AC connection for Ignition Light



If your alternator does not have a D+ connection, you can arrange an ignition light from the AC stator of the alternator. You will require a 12 volt 30amp SPDT automotive relay

Ign Lt set up from AC

15/01/2015 1:05:51 p.m.

Sheet: 1/1